Nama : Aji Mustaqim

NIM : L200180141

PRAKTIKUM KELAS E


PERCOBAAN 4

| AB | | | | |
|----|----|----|----|----|
| CD | 00 | 01 | 11 | 10 |
| | 0 | 1 | 1 | 1 |
| 00 | | | | |
| | 0 | 0 | 1 | 0 |
| 01 | | | | |
| | 0 | 1 | 1 | 0 |
| 11 | | | | |
| | 0 | 0 | 1 | 1 |
| 10 | | | | |

Fungsi Bolean sederhana:

F = AB + AD' + BCD + BC'D'

GAMBAR:

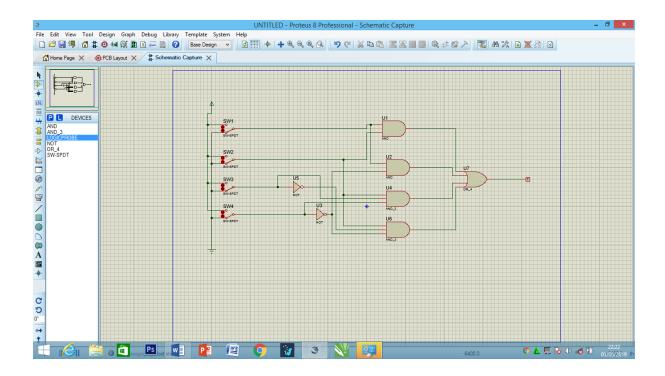


PERCOBAAN 5

| AB | | | | |
|----|----|----|----|----|
| CD | 00 | 01 | 11 | 10 |
| | 1 | 0 | 1 | 0 |
| 00 | | | | |
| | 1 | 0 | 1 | 1 |
| 01 | | | | |
| | 1 | 1 | 0 | 0 |
| 11 | | | | |
| | 1 | 0 | 0 | 1 |
| 10 | | | | |

Fungsi Bolean sederhana:

F = A'B' + A'CD + AC'D + ABC' + B'CD'

GAMBAR

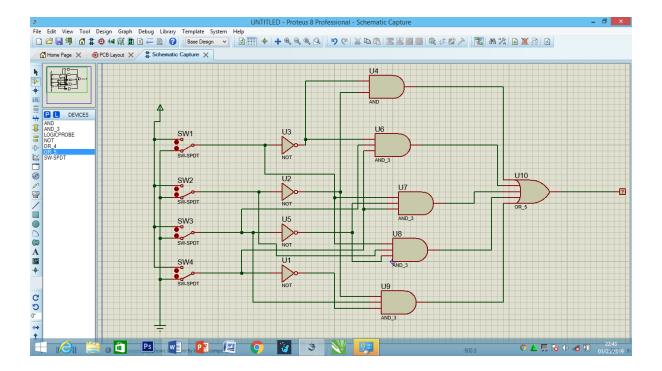

Apakah kedua kombinasi memberikan hasil yang sama? YA